



Multiple Control Constructions

prepared by Maksim Dimitrijevic and Abuzer Yakaryilmaz



```

1 # Because I am running in Android with Google Colab, so I need some cells to be ran every notebook beforehand
2
3 !pip install qiskit==1.3.0
4
5 import qiskit
6 print(qiskit.__version__)
7
8 !pip install pylatexenc
9
10 !pip install qiskit-aer

```

[Show hidden output](#)

Remember that when applying CNOT gate, NOT operator is applied to the target qubit if the control qubit is in state $|1\rangle$:

$$CNOT = \left(\begin{array}{cc|cc} \mathbf{1} & 0 & 0 & 0 \\ 0 & \mathbf{1} & 0 & 0 \\ \hline 0 & 0 & 0 & \mathbf{1} \\ 0 & 0 & \mathbf{1} & 0 \end{array} \right).$$

How can we obtain the following operator, in which the NOT operator is applied to the target qubit if the control qubit is in state $|0\rangle$?

$$C_0NOT = \left(\begin{array}{cc|cc} 0 & \mathbf{1} & 0 & 0 \\ \mathbf{1} & 0 & 0 & 0 \\ \hline 0 & 0 & \mathbf{1} & 0 \\ 0 & 0 & 0 & \mathbf{1} \end{array} \right).$$

As also mentioned in the notebook [Operators on Multiple Bits](#), we can apply a *NOT* operator on the control bit before applying *CNOT* operator so that the *NOT* operator is applied to the target qubit when the control qubit has been in state $|0\rangle$. To recover the previous value of the control qubit, we apply the *NOT* operator once more after the *CNOT* operator. In short:

- apply *NOT* operator to the control qubit,
- apply *CNOT* operator, and,
- apply *NOT* operator to the control qubit.

We can implement this idea in Qiskit as follows.

```

1 from qiskit import QuantumRegister, ClassicalRegister, QuantumCircuit
2 from qiskit_aer import UnitarySimulator
3
4 q = QuantumRegister(2, "q")
5 c = ClassicalRegister(2, "c")
6
7 qc = QuantumCircuit(q, c)
8
9 qc.x(q[1])
10
11 qc.cx(q[1], q[0])
12
13 # Returning control qubit to the initial state
14 qc.x(q[1])
15
16 job = UnitarySimulator().run(qc, shots = 1)
17 U=job.result().get_unitary(qc, decimals=3).data
18
19 print("CNOT(0) = ")
20 for row in U:
21     s = ""

```

```


22     for value in row:
23         s = s + str(round(value.real,2)) + " "
24     print(s)
25
26 qc.draw(output="mpl", reverse_bits=True)

```

```

CNOT(0) =
0.0 1.0 0.0 0.0
1.0 0.0 0.0 0.0
0.0 0.0 1.0 0.0
0.0 0.0 0.0 1.0

```

 

By using this trick, more complex conditional operators can be implemented.

CCNOT

Now we introduce *CCNOT* gate: **controlled-controlled-not operator** ([Toffoli gate](#)), which is controlled by two qubits. The implementation of *CCNOT* gate in Qiskit is as follows:

```
circuit.ccx(control-qubit1, control-qubit2, target-qubit)
```

That is, *NOT* operator is applied to the target qubit when both control qubits are in state $|1\rangle$. Its matrix representation is as follows:


$$CCNOT = \begin{pmatrix} \mathbf{1} & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & \mathbf{1} & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & \mathbf{1} & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & \mathbf{1} & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & \mathbf{1} & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & \mathbf{1} & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & \mathbf{1} \\ 0 & 0 & 0 & 0 & 0 & 0 & \mathbf{1} & 0 \end{pmatrix}.$$

Task 1

Implement each of the following operators in Qiskit by using three qubits. Verify your implementation by using "unitary_simulator" backend.


$$C_0C_0NOT = \begin{pmatrix} 0 & \mathbf{1} & 0 & 0 & 0 & 0 & 0 & 0 \\ \mathbf{1} & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & \mathbf{1} & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & \mathbf{1} & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & \mathbf{1} & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & \mathbf{1} & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & \mathbf{1} & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & \mathbf{1} \end{pmatrix}, \quad C_0C_1NOT = \begin{pmatrix} \mathbf{1} & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & \mathbf{1} & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & \mathbf{1} & 0 & 0 & 0 & 0 \\ 0 & 0 & \mathbf{1} & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & \mathbf{1} & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & \mathbf{1} & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & \mathbf{1} & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & \mathbf{1} \end{pmatrix}, \quad \text{and } C_1C_0NOT = \begin{pmatrix} \mathbf{1} & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & \mathbf{1} & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & \mathbf{1} & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & \mathbf{1} & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & \mathbf{1} & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & \mathbf{1} & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & \mathbf{1} & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & \mathbf{1} \end{pmatrix}.$$

1 Start coding or [generate](#) with AI.

 


CNOT(00) =

0.0	1.0	0.0	0.0	0.0	0.0	0.0	0.0
1.0	0.0	0.0	0.0	0.0	0.0	0.0	0.0
0.0	0.0	1.0	0.0	0.0	0.0	0.0	0.0
0.0	0.0	0.0	1.0	0.0	0.0	0.0	0.0
0.0	0.0	0.0	0.0	1.0	0.0	0.0	0.0
0.0	0.0	0.0	0.0	0.0	1.0	0.0	0.0
0.0	0.0	0.0	0.0	0.0	0.0	1.0	0.0
0.0	0.0	0.0	0.0	0.0	0.0	0.0	1.0

 

CNOT(01) =

1.0	0.0	0.0	0.0	0.0	0.0	0.0	0.0
0.0	1.0	0.0	0.0	0.0	0.0	0.0	0.0
0.0	0.0	0.0	1.0	0.0	0.0	0.0	0.0
0.0	0.0	1.0	0.0	0.0	0.0	0.0	0.0
0.0	0.0	0.0	0.0	1.0	0.0	0.0	0.0
0.0	0.0	0.0	0.0	0.0	1.0	0.0	0.0
0.0	0.0	0.0	0.0	0.0	0.0	1.0	0.0
0.0	0.0	0.0	0.0	0.0	0.0	0.0	1.0

 

CNOT(10) =

1.0	0.0	0.0	0.0	0.0	0.0	0.0	0.0
0.0	1.0	0.0	0.0	0.0	0.0	0.0	0.0
0.0	0.0	0.0	1.0	0.0	0.0	0.0	0.0
0.0	0.0	0.0	0.0	0.0	1.0	0.0	0.0
0.0	0.0	0.0	0.0	0.0	0.0	1.0	0.0
0.0	0.0	0.0	0.0	0.0	0.0	0.0	1.0
0.0	0.0	0.0	0.0	0.0	0.0	0.0	0.0
0.0	0.0	0.0	0.0	0.0	0.0	0.0	0.0

[click for our solution](#)

Double click (or enter) to edit

1 Start coding or [generate](#) with AI.

More controls

Here we present basic methods on how to implement *NOT* gates controlled by more than two qubits by using *CNOT*, *CCNOT*, and some ancilla (auxiliary) qubits.


(Note that Qiskit has a method called "mct" to implement such gates. Another multiple-controlled operator in Qiskit is "mcrz".)

Implementation of CCCNOT gate

We give the implementation of *CCCNOT* gate: *NOT* operator is applied to target qubit when the control qubits are in state $|111\rangle$. This gate requires 4 qubits. We also use an auxiliary qubit.

Our qubits are q_{aux} , q_3 , q_2 , q_1 , q_0 , and the auxiliary qubit q_{aux} should be in state $|0\rangle$ after each use. The implementation of the *CCCNOT* gate in Qiskit is given below. The short explanations are given as comments.

```
1 from qiskit import QuantumRegister, ClassicalRegister, QuantumCircuit
2 from qiskit_aer import AerSimulator
3
4 qaux = QuantumRegister(1,"qaux")
5 q = QuantumRegister(4,"q")
6 c = ClassicalRegister(4,"c")
7
8 qc = QuantumCircuit(q,qaux,c)
9
10 # step 1: set qaux to |1> if both q3 and q2 are in |1>
11 qc.ccx(q[3],q[2],qaux[0])
12
13 # step 2: apply NOT gate to q0 if both qaux and q1 are in |1>
14 qc.ccx(qaux[0],q[1],q[0])
15
16 # step 3: set qaux to |0> if both q3 and q2 are in |1> by reversing the affect of step 1
17 qc.ccx(q[3],q[2],qaux[0])
18
19 qc.draw(output="mpl",reverse_bits=True)
```

 

Now, we execute this circuit on every possible inputs and verify the correctness of the implementation experimentally.

```
1 from qiskit import QuantumRegister, ClassicalRegister, QuantumCircuit
2 from qiskit_aer import AerSimulator
3
4 all_inputs=[]
5 for q3 in ['0','1']:
6     for q2 in ['0','1']:
7         for q1 in ['0','1']:
8             for q0 in ['0','1']:
9                 all_inputs.append(q3+q2+q1+q0)
10 #print(all_inputs)
11
```

```

12 print("input --> output")
13 for the_input in all_inputs:
14     # create the circuit
15     qaux = QuantumRegister(1,"qaux")
16     q = QuantumRegister(4,"q")
17     c = ClassicalRegister(4,"c")
18     qc = QuantumCircuit(q,qaux,c)
19     # set the initial value of the circuit w.r.t. the input
20     if the_input[0] == '1': qc.x(q[3])
21     if the_input[1] == '1': qc.x(q[2])
22     if the_input[2] == '1': qc.x(q[1])
23     if the_input[3] == '1': qc.x(q[0])
24     # implement the CCNOT gates
25     qc.ccx(q[3],q[2],qaux[0])
26     qc.ccx(qaux[0],q[1],q[0])
27     qc.ccx(q[3],q[2],qaux[0])
28     # measure the main quantum register
29     qc.measure(q,c)
30     # execute the circuit
31     job = AerSimulator().run(qc,shots=1)
32     counts = job.result().get_counts(qc)
33     for key in counts: the_output = key
34     printed_str = the_input[0:3]+" "+the_input[3]+" --> "+the_output[0:3]+" "+the_output[3]
35     if (the_input!=the_output): printed_str = printed_str + " the output is different than the input"
36     print(printed_str)

```

```

['0000', '0001', '0010', '0011', '0100', '0101', '0110', '0111', '1000', '1001', '1010', '1011', '1100', '1101', '1110', '1111']
input --> output
000 0 --> 000 0
000 1 --> 000 1
001 0 --> 001 0
001 1 --> 001 1
010 0 --> 010 0
010 1 --> 010 1
011 0 --> 011 0
011 1 --> 011 1
100 0 --> 100 0
100 1 --> 100 1
101 0 --> 101 0
101 1 --> 101 1
110 0 --> 110 0
110 1 --> 110 1
111 0 --> 111 1 the output is different than the input
111 1 --> 111 0 the output is different than the input

```

Task 2

Provide an implementation of the NOT operator controlled by 4 qubits ($CCCCNOT$) in Qiskit. Verify its correctness by executing your solution on all possible inputs. (See the above example)

You may use two auxiliary qubits.

[click for our solution](#)

Task 3

Repeat Task 2 for the operator $C_1C_0C_1C_0NOT$: NOT operator is applied to the target qubit if the four control qubits are in state $|1010\rangle$.

[click for our solution](#)

Task 4 (extra)

Write a function taking a binary string $b_1b_2b_3b_4$ that repeats Task 2 for the operator $C_{b_1}C_{b_2}C_{b_3}C_{b_4}NOT$ gate, where b_1, \dots, b_4 are bits and NOT operator is applied to target qubit if the control qubits are in state $|b_1b_2b_3b_4\rangle$.

[click for our solution](#)